


ALTERNATING CURRENT: A VISUAL REVISION GUIDE

AC vs. DC: THE FUNDAMENTALS

Direct Current (DC)

Flows in one direction.

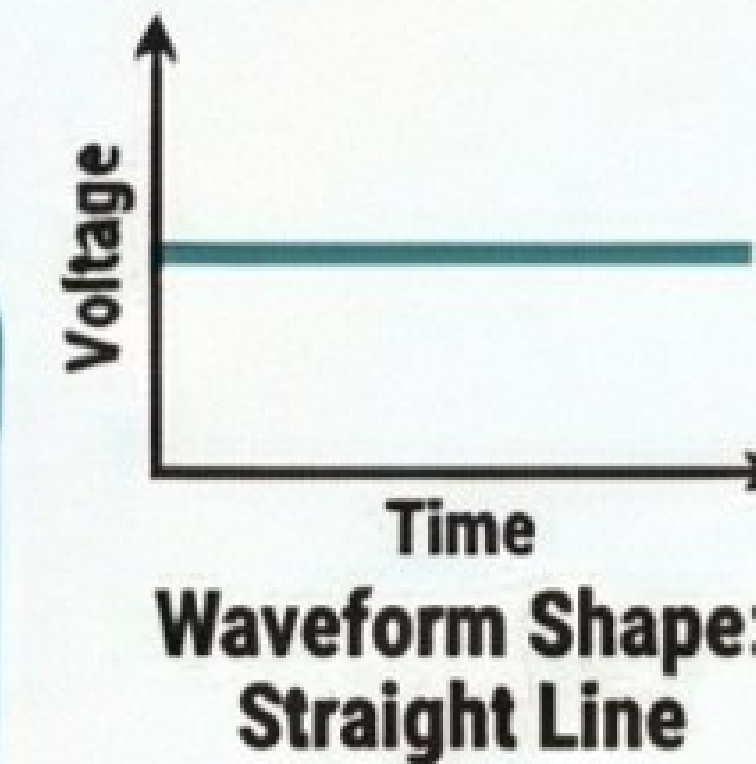
In DC, the magnitude and direction of current are constant, meaning electrons flow steadily in a single direction.



Alternating Current (AC)

Periodically reverses direction.

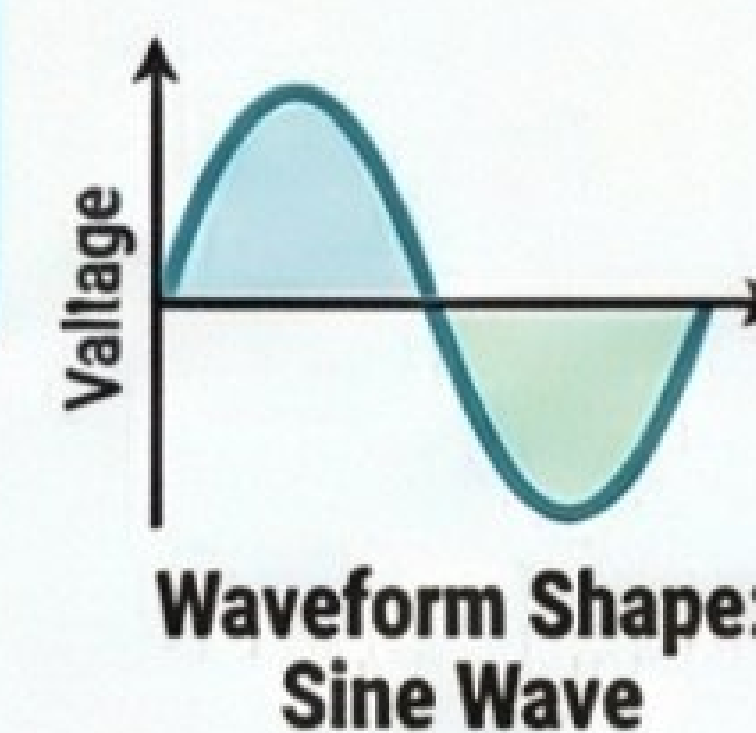In AC, electrons oscillate back and forth. The magnitude changes continuously, while the direction reverses after a fixed time interval.




Frequency in India is 50 Hz for AC. This means one, the frequency of DC is always 0 Hz.

UNDERSTANDING AC VALUES: PEAK vs. RMS

I_0 (Peak Value)

RMS value is the 'effective' value of AC. The RMS (Root Mean Square) value of an AC current is the equivalent DC current that would produce the same amount of heat in the same resistor.

I_{rms} (Effective Value)

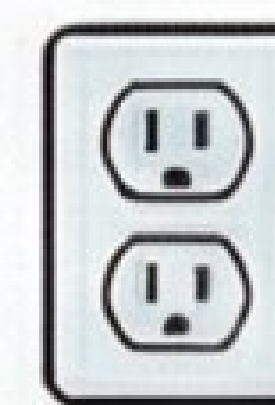

Household ratings are RMS values. If a device label says 10A AC, it refers to the RMS value, not the maximum (peak) current.

Relating RMS and Peak Values:


$$I_{rms} = \frac{I_0}{\sqrt{2}}$$



220V AC is more dangerous than 220V DC. A 220V DC shock is constant at 220V. For 220V AC (which is the RMS value), the peak voltage reaches $220V \times \sqrt{2} \approx 311V$, delivering a more severe shock.




KEY AVERAGES & DERIVATIONS

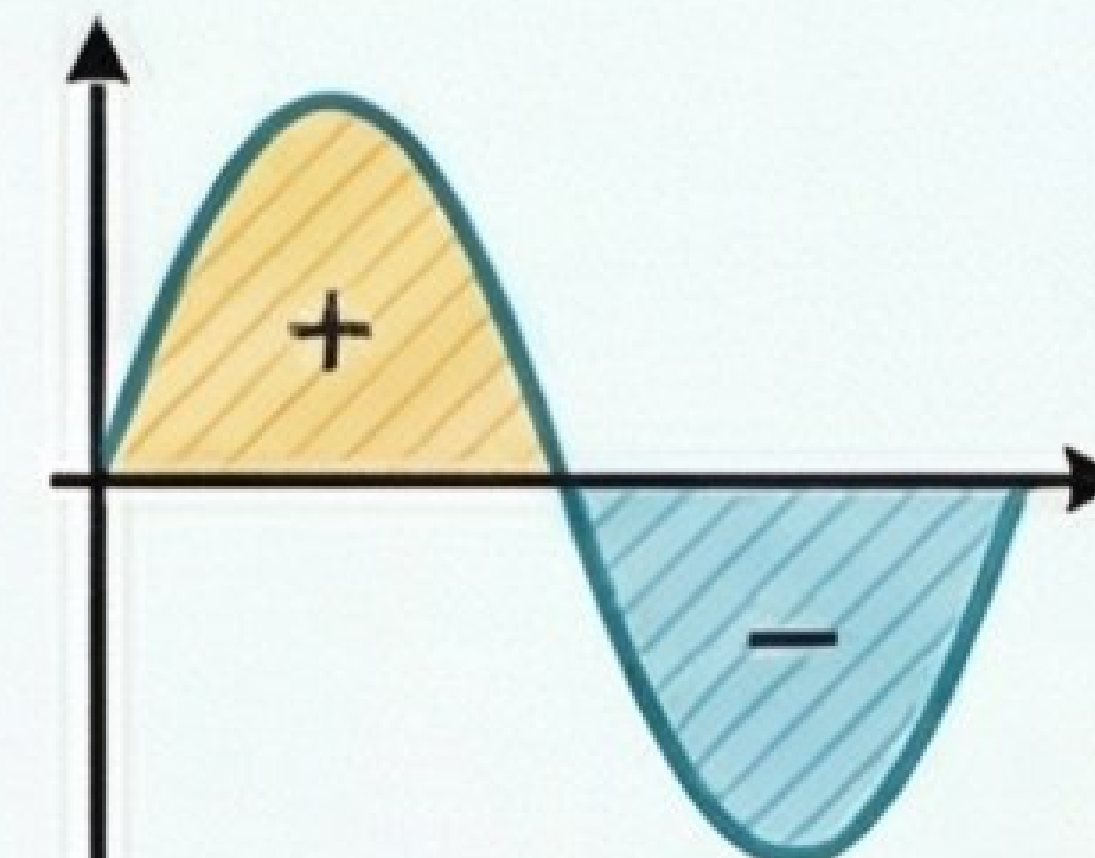

Average current over a full cycle is ZERO.

The positive half-cycle cancels out the negative half-cycle, resulting in a net average value of zero.

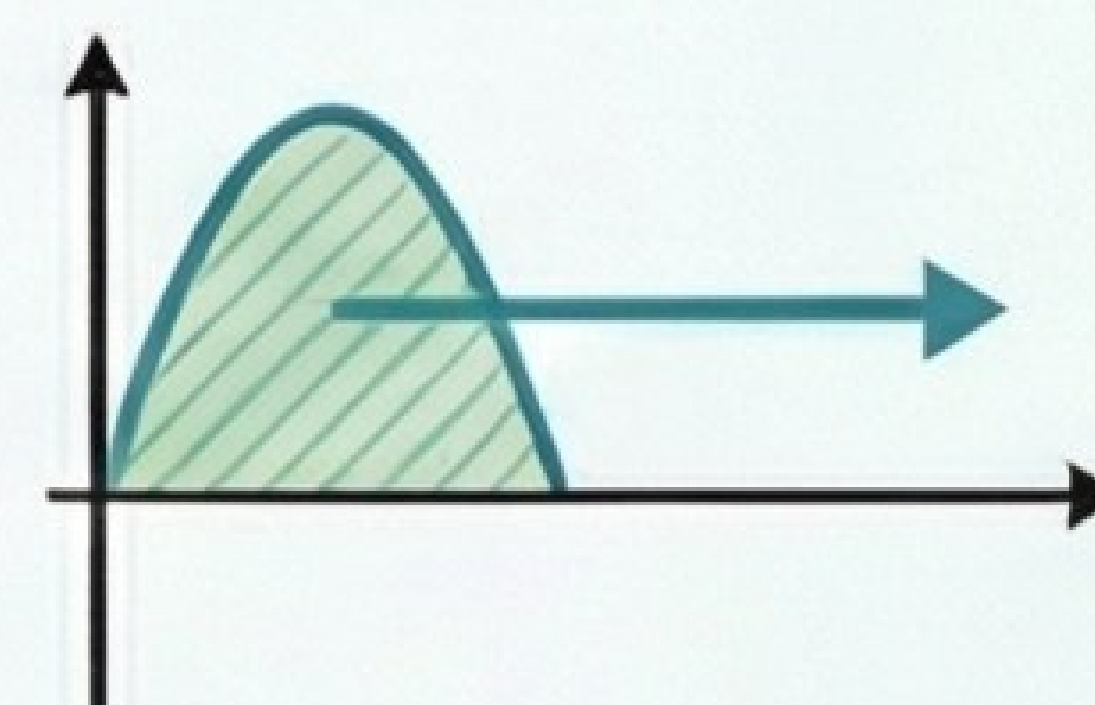This is why AC doesn't produce a chemical effect.



Average current over a half cycle is not zero.

Formula: $I_{avg} = 0$

The total charge transferred over one complete cycle is zero.


ESSENTIAL AC DEVICES & CIRCUITS

LCR CIRCUIT & IMPEDANCE

In a series circuit with a resistor (R), inductor (L), and capacitor (C), the total opposition to current is called impedance (Z).

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


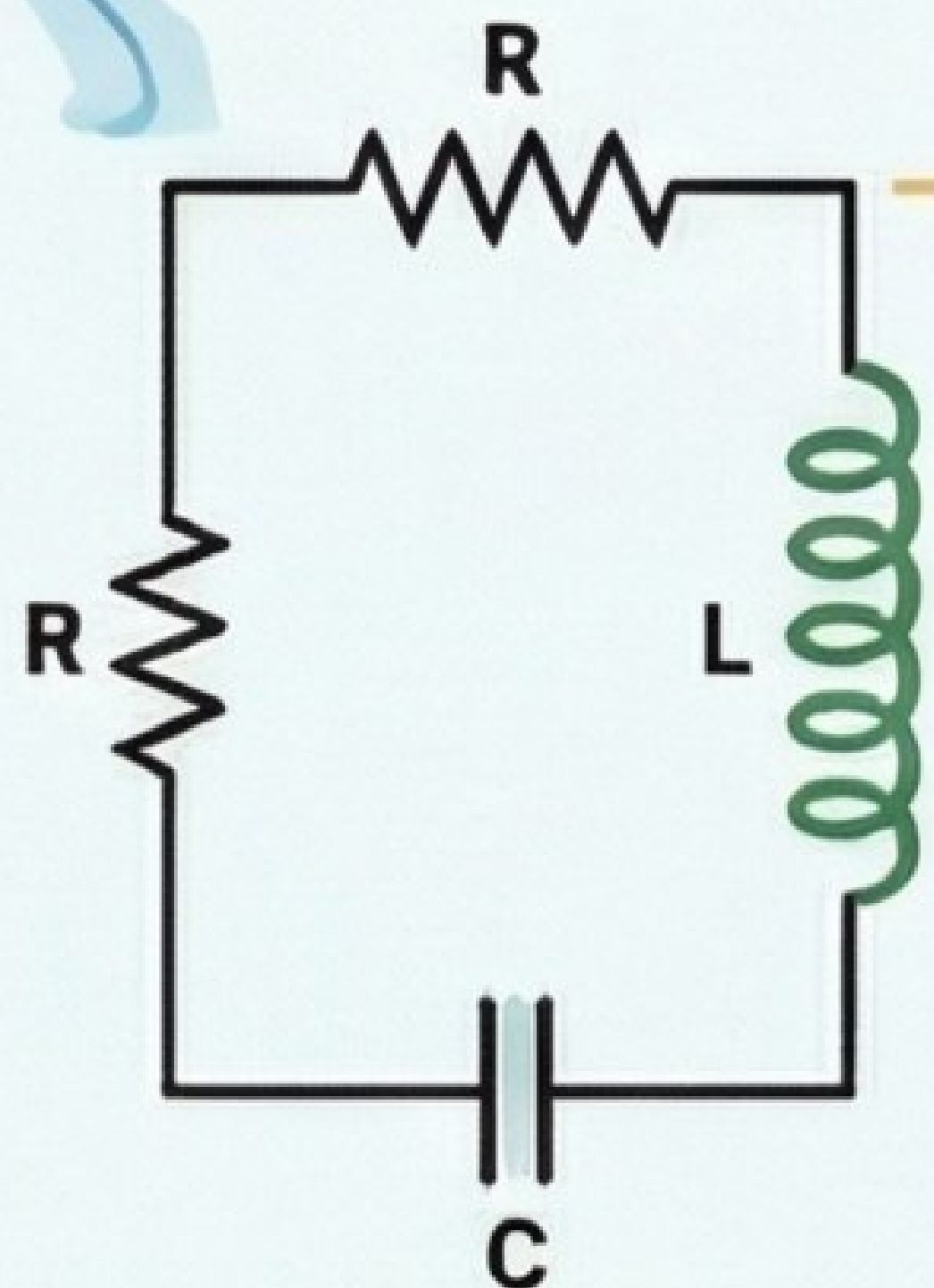
Electrical Resonance: Resonance occurs when the circuit's impedance is at its minimum ($Z=R$), allowing maximum current to flow. This happens when inductive reactance (X_L) equals capacitive reactance (X_C).



CHOKE COIL

Controls current efficiently.

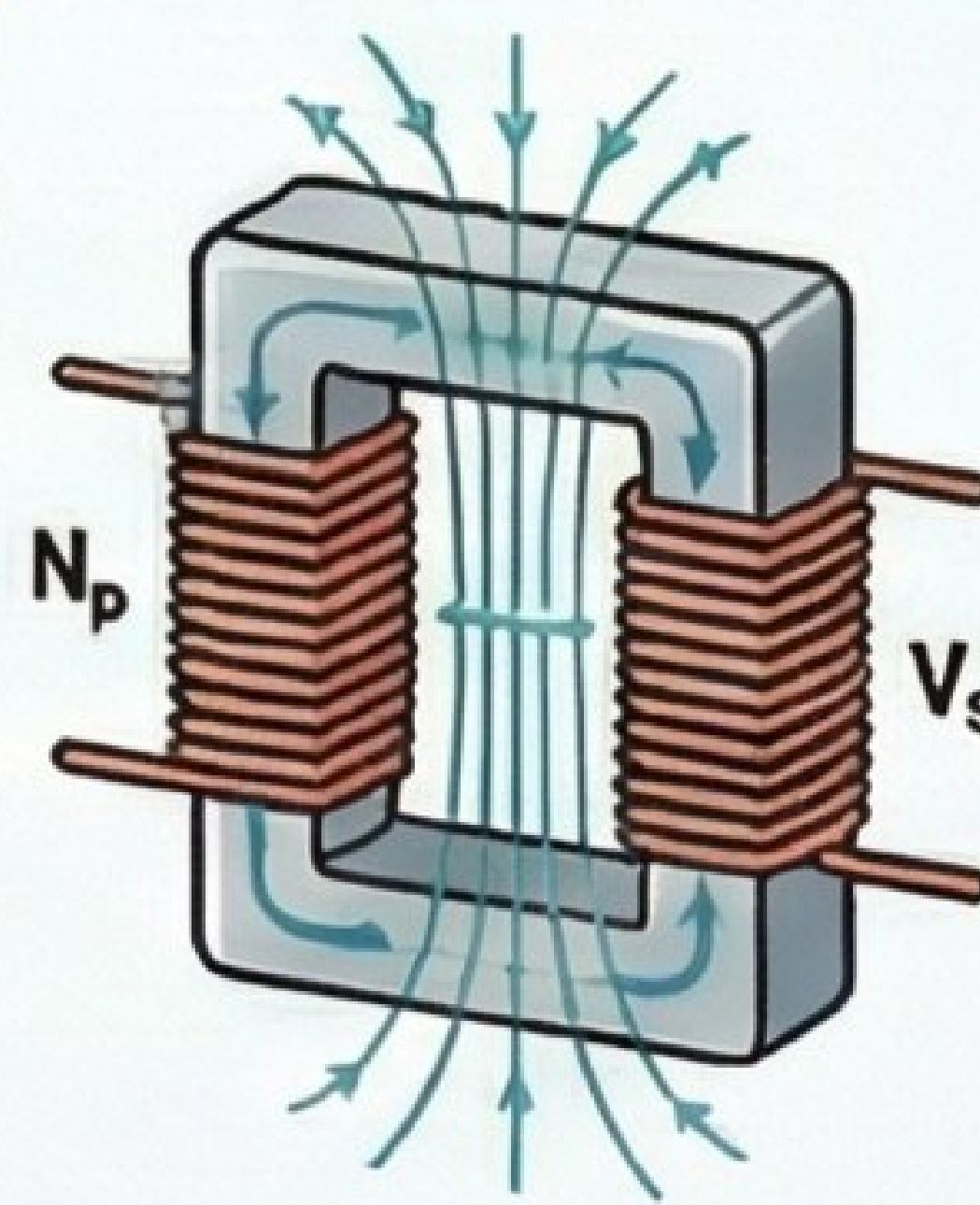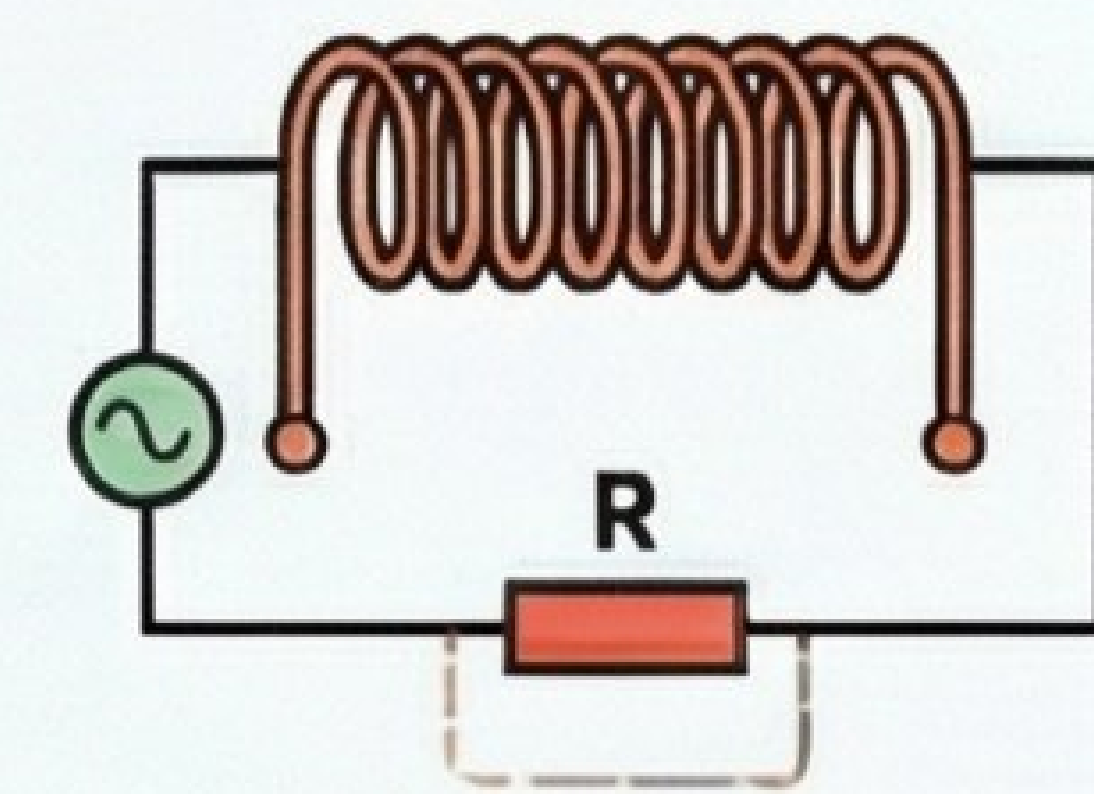
A choke coil is an inductor used to control AC with minimal power loss, as it opposes current via self-induction rather than dissipating energy as heat like a resistor.



TRANSFORMER

Changes AC voltage levels.

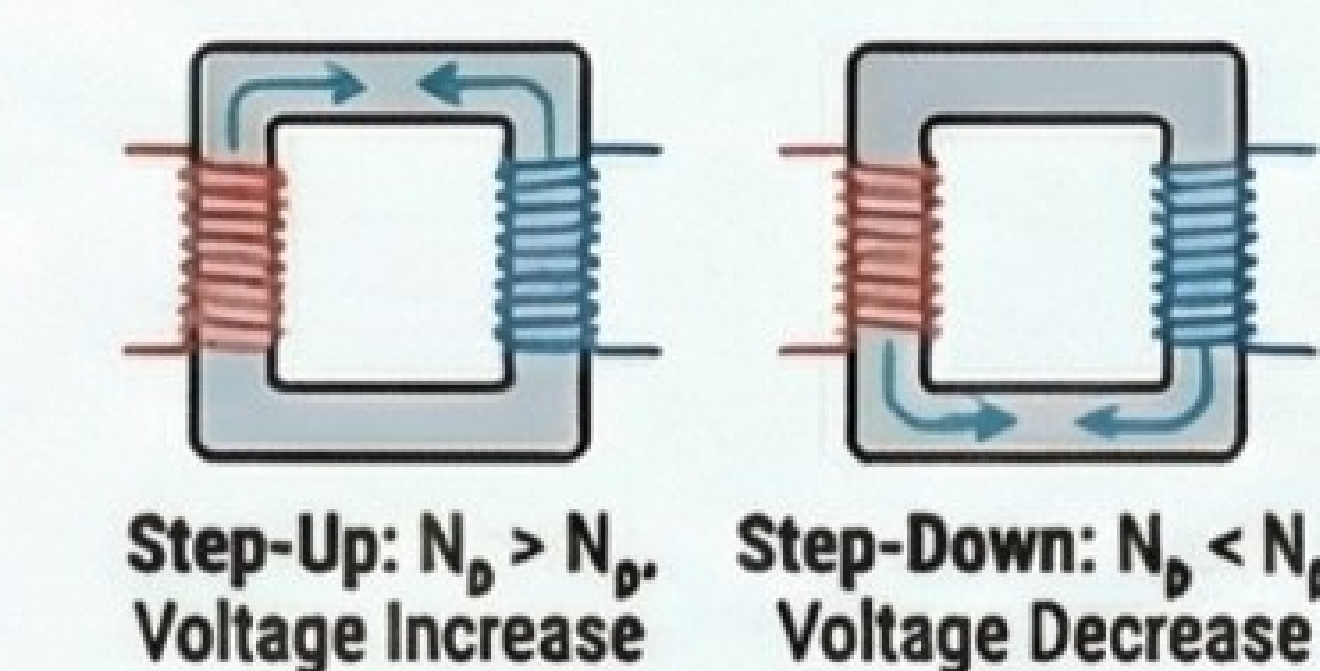Working on the principle of mutual induction, a transformer can increase (step-up) or decrease (step-down) AC voltage. It does not work with DC.




Transformers conserve power. In an ideal transformer, input power equals output power ($V_p I_p = V_s I_s$).

AC GENERATOR

Converts mechanical to electrical energy.

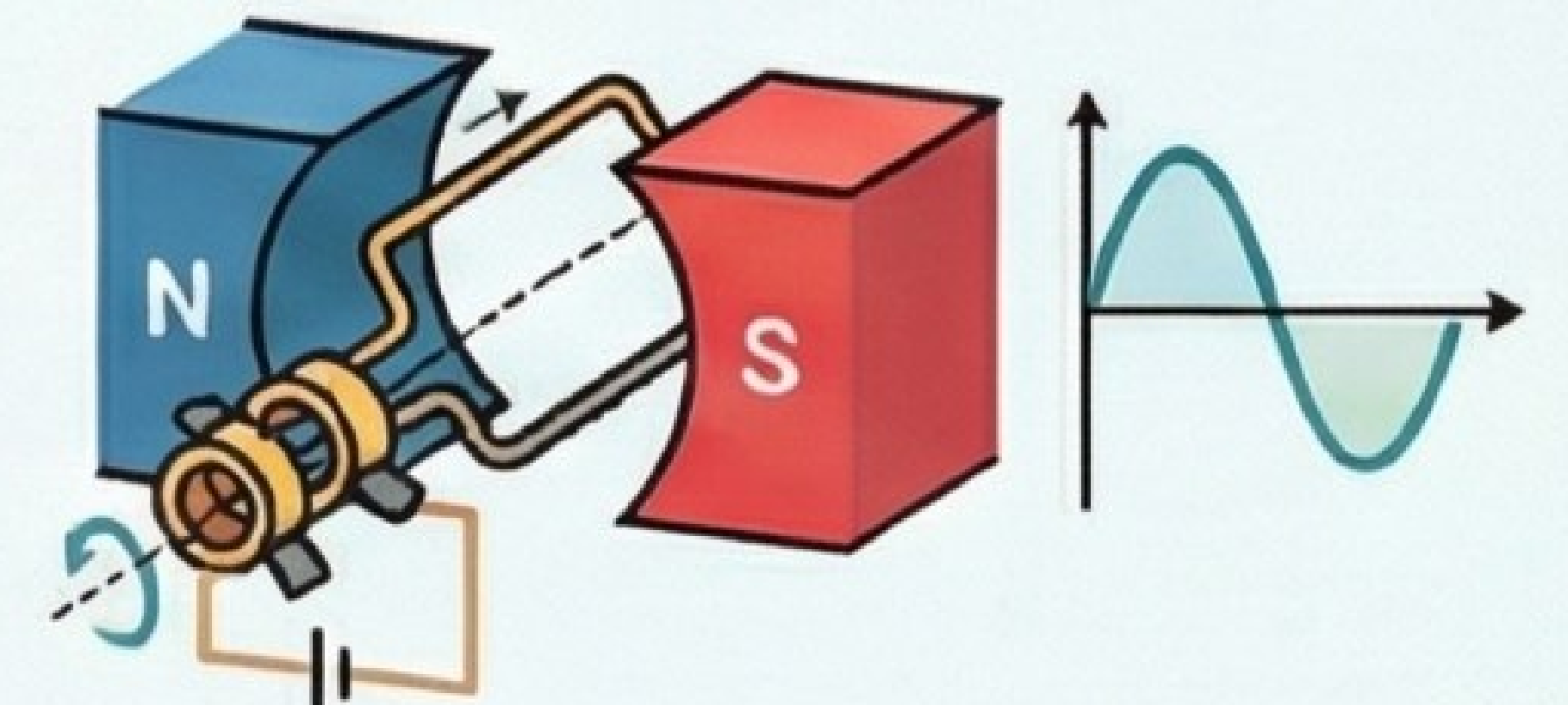Based on the principle of electromagnetic induction, it generates AC by rotating a coil in a magnetic field, which continuously changes the magnetic flux.



How it Works: As the coil rotates, the direction of the induced current (determined by Fleming's Right-Hand Rule) reverses every half rotation, creating alternating current.